



Orcad Advanced Workshop

GABRIEL CHAN


Overview

- ▶ CMOS and TTL
- ▶ BJT Transistors – 2N3904(NPN) and 2N3906(PNP)
- ▶ Darlington Transistors – TIP122(NPN) and TIP127(PNP)
- ▶ MOSFETS – IRF840(NMOS) and IRF9510(PMOS)

CMOS


- ▶ Stands for **C**omplementary **m**etal-**o**xide – **s**emiconductor
- ▶ Logic High = 3.3V
- ▶ Logic Low = 0V

TTL

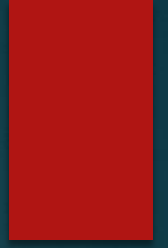

- ▶ Stands for **T**ransistor-**T**ransistor **L**ogic
- ▶ Logic High 2V – 4.95V
- ▶ Logic Low 0 V – 0.8V

NPN 2N3904

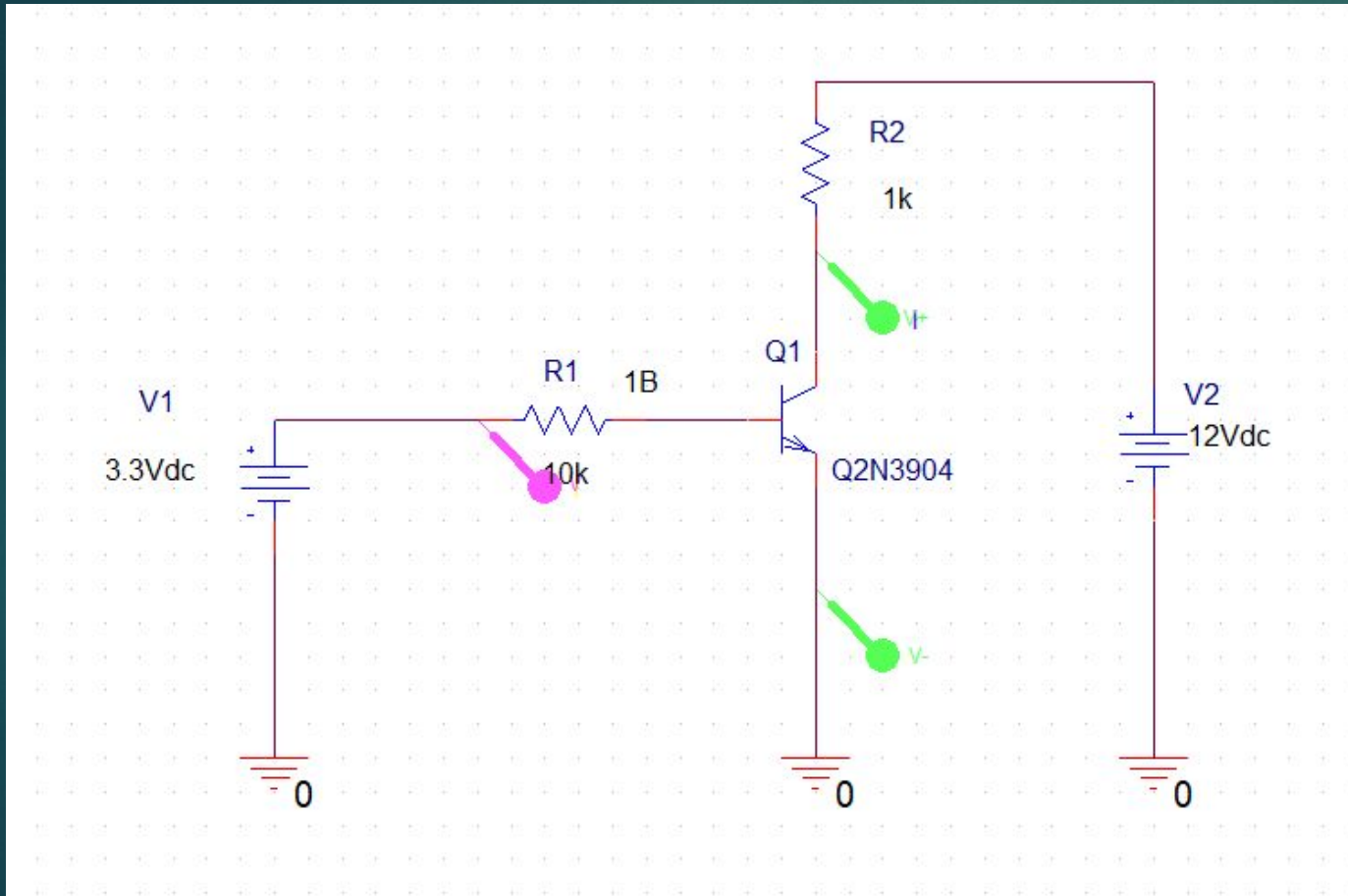

Find I_C and V_{CE} when $V_{BB} = 3.3V$

$$I_B = (V_{BB} - V_{BE})/R_B$$

$$= (3.3 - 0.7)/10k$$

$$= 260\mu A$$

$$I_C = \beta(I_B)$$

$$= 100(260nA)$$

$$= 26mA$$

$$V_{CE} = V_{CC} - I_C R_C$$

$$= 12V - (26mA)(1k)$$

$$= -14V(\text{impossible oversaturated})$$

Find I_C and V_{CE} when $V_{BB} = 0V$

$$I_B = (V_{BB} - V_{BE})/R_B$$

$$= (0 - 0.7)/10k$$

$$= -70\mu A$$

$$I_C = \beta(I_B)$$

$$= 100(-70nA)$$

$$= -7mA$$

$$V_{CE} = V_{CC} - I_C R_C$$

$$= 12V - (-7mA)(1k)$$

$$= 19(\text{also impossible cutoff})$$

Cut Off vs Saturation

Saturation	Cutoff
$V_{CE} = 0$ $I_C = V_{CC}/R_C$	$V_{CE} = V_{CC}$ $I_C = 0$

PNP 2N3906

Find I_C and V_{CE} when $V_{BB} = 0V$

$$I_B = (V_{EE} - V_{BB} - V_{BE}) / R_B$$

$$= (12 - 0 - 0.7) / 10k$$

$$= 1.13mA$$

$$I_C = \beta * I_B$$

$$= 113mA$$

$$V_{CE} = V_{EE} - I_C R_C$$

$$= 12 - (113mA * 1k)$$

= -101 (impossible oversaturated)

Find I_C and V_{CE} when $V_{BB} = 13V$

$$I_B = (V_{EE} - V_{BB} - V_{BE}) / R_B$$

$$= (12 - 13 - 0.7) / 10k$$

$$= -170\mu A$$


$$I_C = \beta * I_B$$

$$= -17mA$$

$$V_{CE} = V_{EE} - I_C R_C$$

$$= 12 - (-17mA * 1k)$$

= 29 (impossible cutoff)

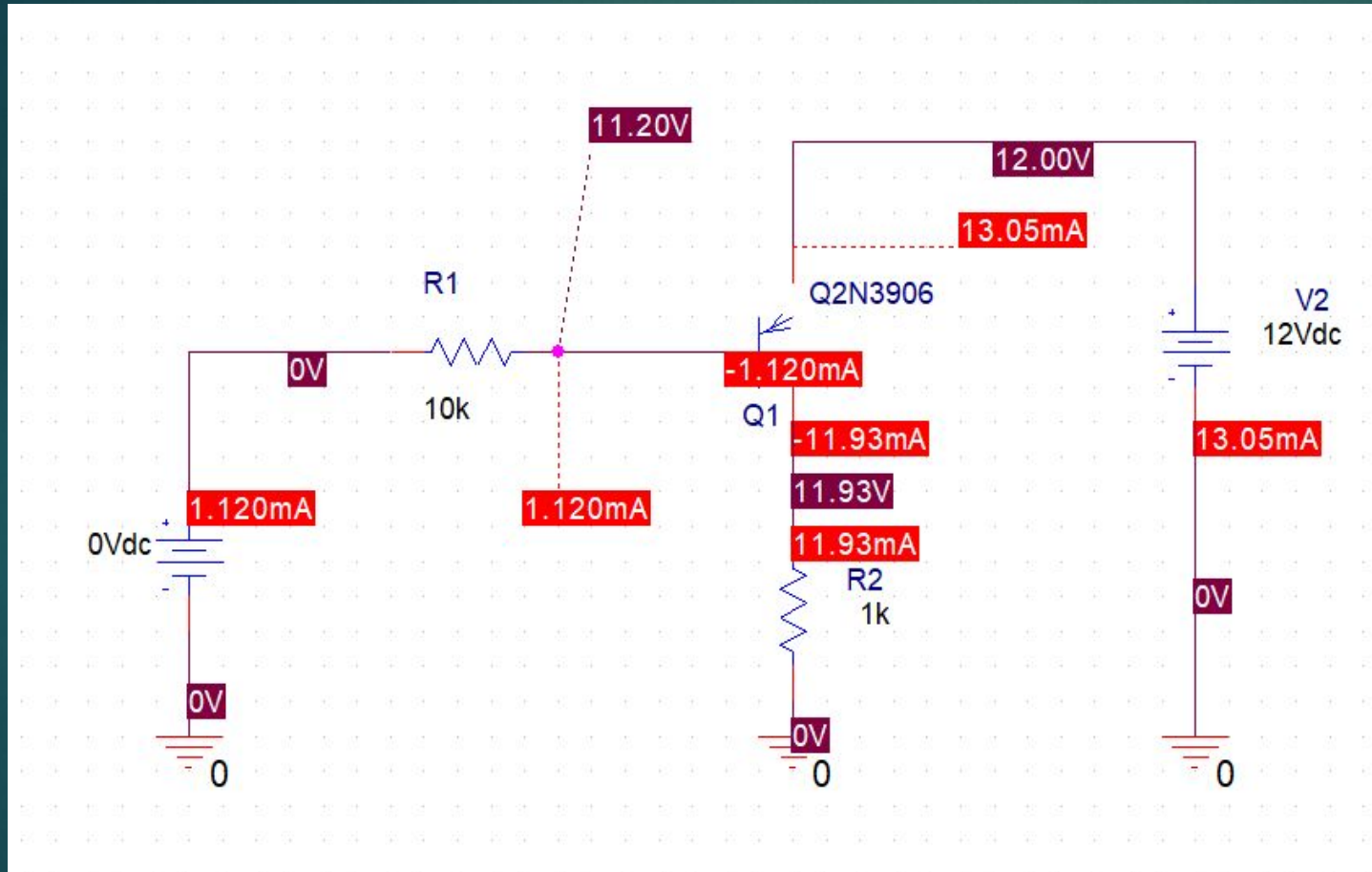


Adding library files into OrCAD

- ▶ Find .OLB and .LIB versions of your library files
- ▶ Add or overwrite .lib file into
C:\OrCAD\OrCAD_16.6_Lite\tools\pspice\library
- ▶ Add or overwrite .olb file into
C:\OrCAD\OrCAD_16.6_Lite\tools\capture\library\pspice

NMOS IRF840

Threshold for IRF840 = 3.879V

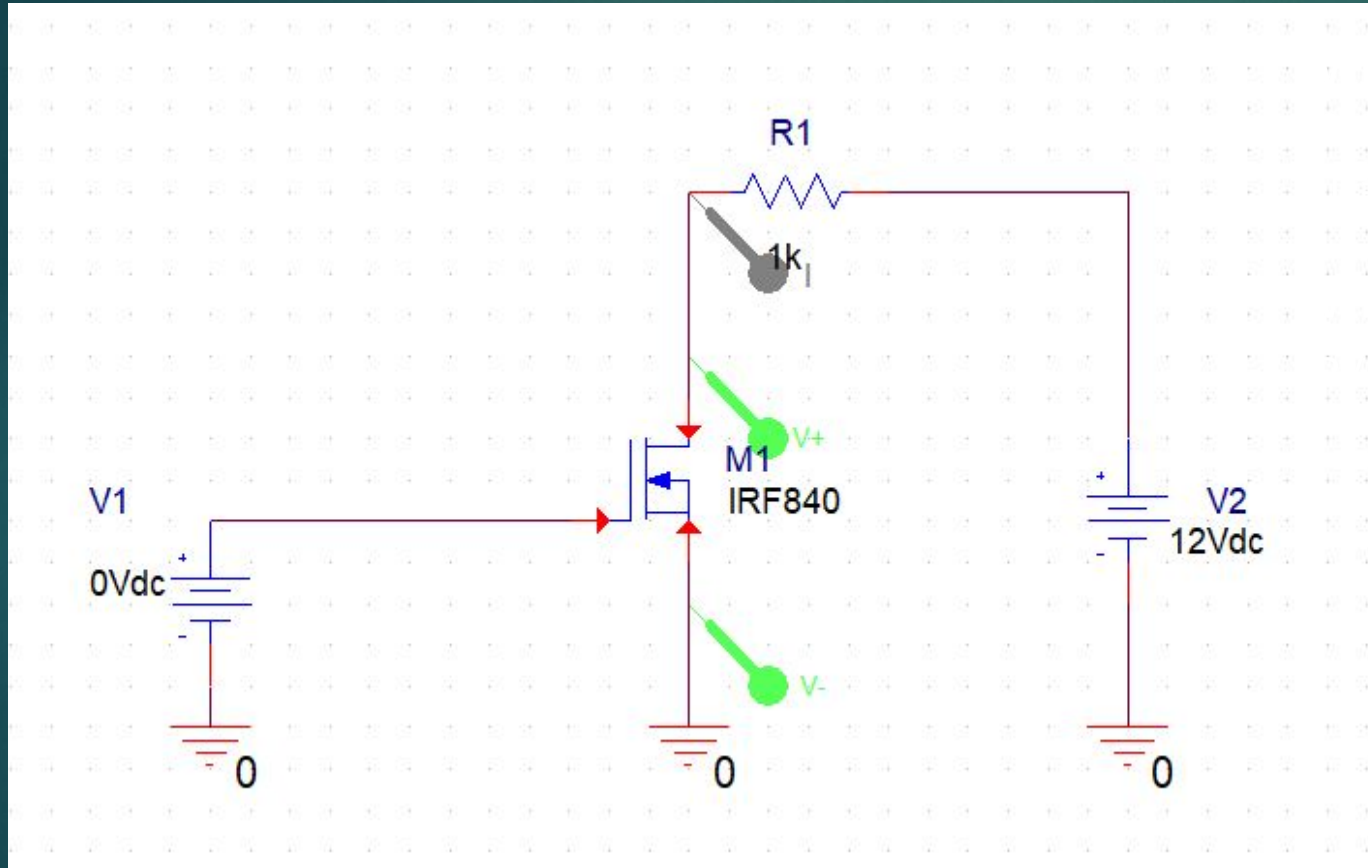

When $V_G = 0V$

$V_G < 3.879V$


$I_D = V_2/R_1 = 12V/1k = 12mA$ (cutoff)

When $V_G = 5V$

$V_G > 3.879V$

$I_D = 0V/1k = 0mA$ (saturated)

IRF9510

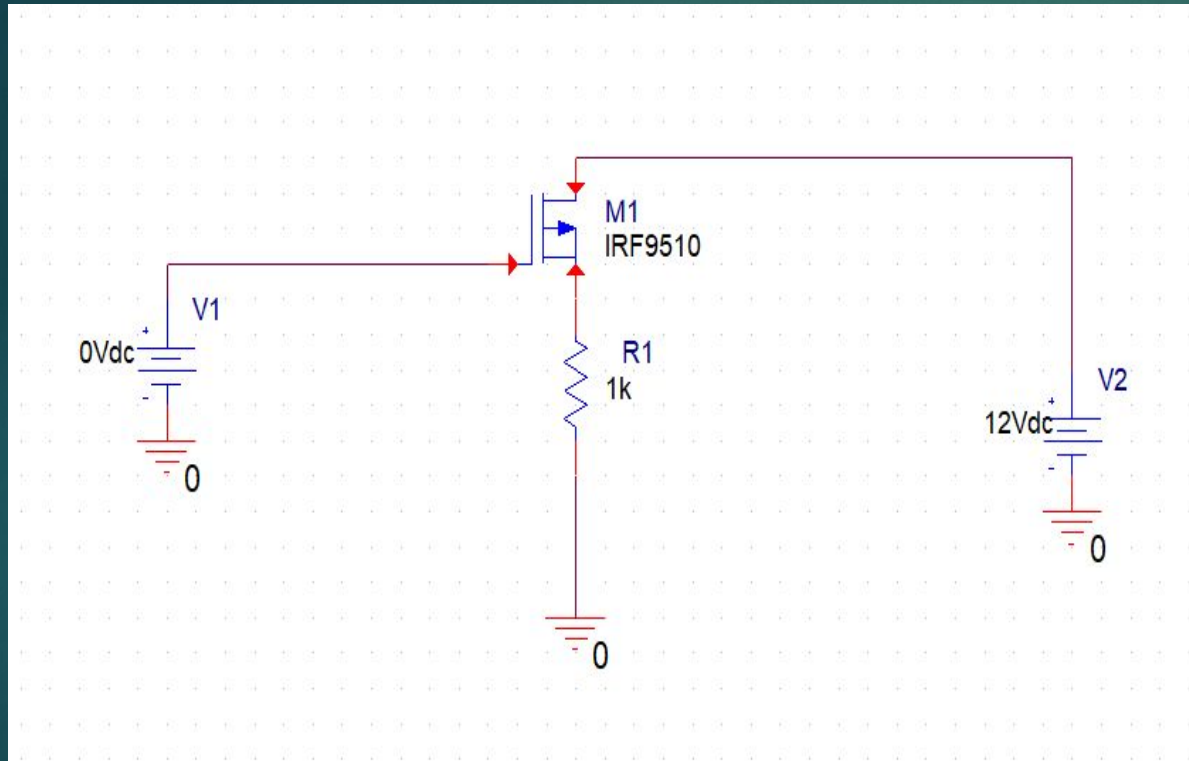

Threshold for IRF9510 = -3.9V

When $V_G = 0V$

$$V_{GS} = V_G - V_s = 0 - 12V = -12V$$


$$I_L = V_2/R_1 = 0V/1k = 0mA(\text{saturated})$$

When $V_G = 12V$

$$V_{GS} = V_G - V_s = 12 - 12V = 0V$$

$$I_L = V_2/R_1 = 12V/1k = 12mA(\text{cutoff})$$

Level Shifting with IRF840

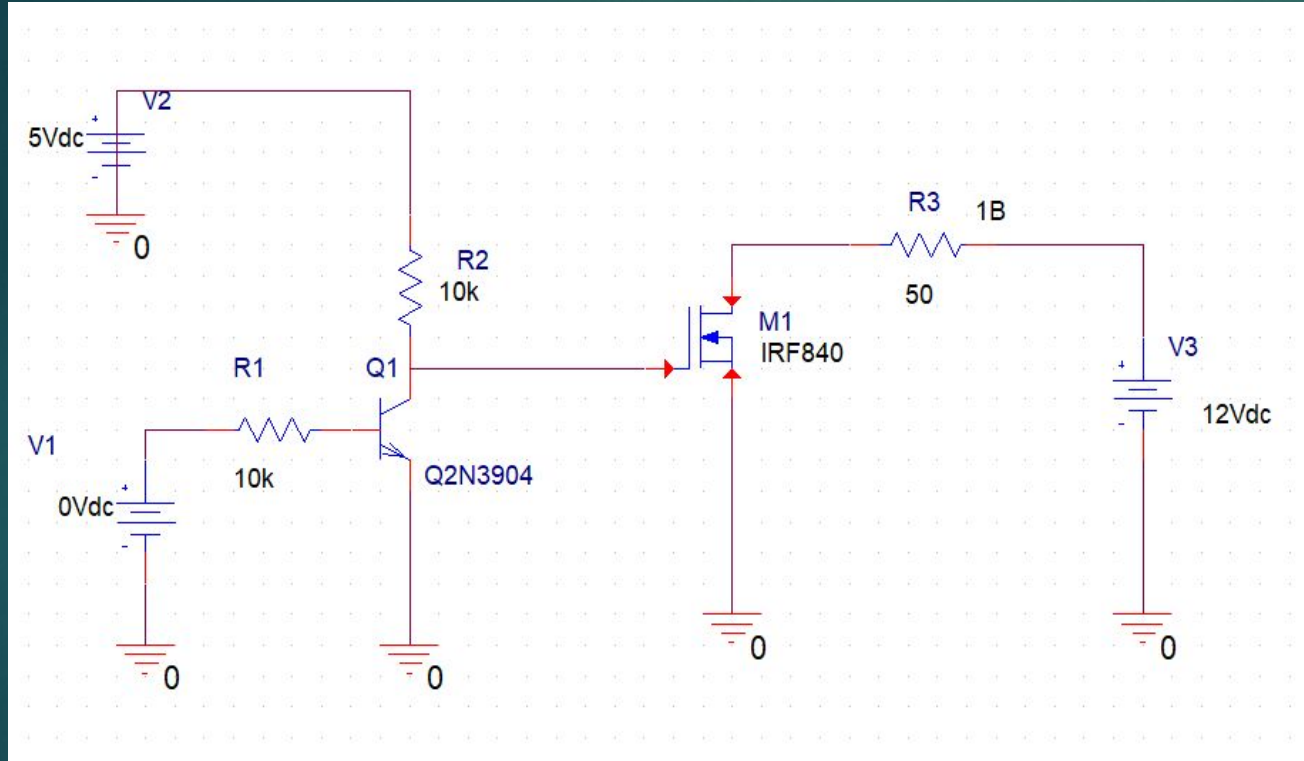

When input is Logic 1 = 3.3V

$$I_{R1} = (V1 - V_{BE}) / R1$$

$$= (3.3 - 0.7) / 10k$$

$$= 260\mu A$$

$$I_{R2} = \beta * I_{R1}$$

$$= 26mA$$

$$V_{CE} = V2 - (I_{R2} * R2)$$

$$= 5 - (26mA * 10k)$$

$$= -248 \text{ (same as } V_{CE} = 0 \text{ - oversaturated)}$$

0V will go into IRF840

$$I_{R3} = V3 / R3$$

$$= 12 / 50$$

$$= 240mA \text{ (cutoff)}$$